

(Set-1)

B.Tech - 4th
AdEC

Full Marks : 70

Time : 3 hours

**Q. No. 1 is compulsory and answer any
five from the rest**

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2×10

- (a) What is an active filter ? Draw and explain a band stop filter.
- (b) Explain the operation of a universal active filter.
- (c) Differentiate between a comparator and a saw tooth wave generator.
- (d) Write two applications of an instrumentation amplifier.

(Turn Over)

- (e) Why compensation is necessary in wideband amplifiers ?
- (f) What do you mean by stable states of a binary ?
- (g) Discuss the role of commutating capacitor in bistable multivibrator.
- (h) What are the operating modes of IC 555 timer ?
- (i) Draw the block diagram of a voltage controlled oscillator.
- (j) Write down some applications of voltage time base generator.
2. (a) Draw and explain the principle of operation of low pass, high pass, band pass and band reject filters.
- (b) A step input of 10 V when applied to the low pass RC circuit produces the output with a rise time of 200 μ S. Calculate the upper 3dB

- frequency of the circuit if the circuit uses a capacitor of 0.47 μ F. Determine the value of the resistance.
3. (a) Draw and explain the operation of instrumentation amplifier circuit. What is the expression for its voltage output ?
- (b) Design a wideband filter with $f_l = 400$ Hz and $f_h = 2$ KHz and passband gain of 4. Calculate Q for the filter and comment on the result.
4. (a) Describe the triggering mechanism for a bistable multivibrator with suitable diagrams.
- (b) Draw and explain the Schmitt trigger circuit.
5. (a) Draw and explain the principle of operation of an emitter coupled astable multivibrator.
- (b) Explain how tunnel diode can be used as monostable, astable multivibrator.

6. (a) Explain the principle of operation of a voltage time base generator. Discuss about its applications. 5
- (b) Explain the operation of a current time base generator circuit with applications. 5
7. (a) Draw and explain the block diagram of a PLL circuit. Discuss about its applications. 5
- (b) Explain the operation of IC 555 timer circuit and its applications. 5
8. Write short notes on any two : 5×2
- (i) Sawtooth wave generation using UJT
- (ii) VOC using IC 555 timer
- (iii) Shunt compensation
- (iv) Triangular wave generator.
-