
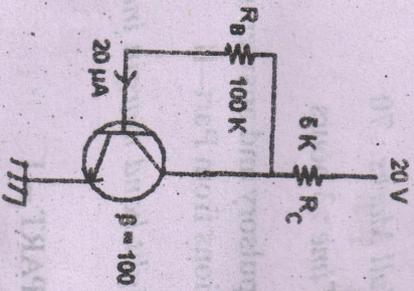


( 2 )

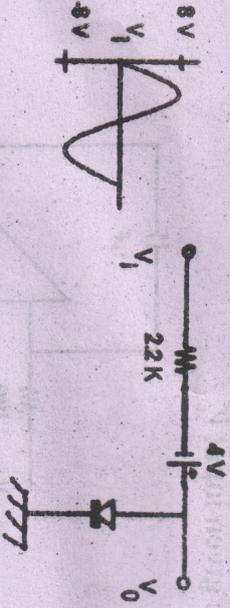- (b) Determine the collector to emitter voltage ( $V_{CE}$ ) of the following circuit




- (c) Determine  $V_o$  for a sinusoidal input  $V_i$  of amplitude 8 Volts



- (d) Simplify the following Boolean expression  
 $A(A + B)X + A + C(XA + B + C)$

( 3 )

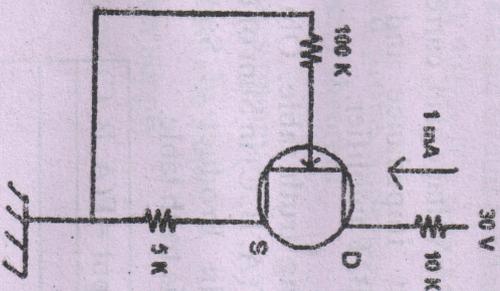- (e) Realize all others gates using NOR gate.  
(f) Determine the decimal equivalent of  
(i) (100101.01101)<sub>2</sub>  
(ii) (25.3)<sub>8</sub>  
(g) Determine  $V_{DS}$  from the following JFET circuit



- (h) Can you construct an RC oscillator with a two stage of RC network ? Justify.  
(i) Design the circuit of a scale of 4 counter using JK Flip-flop.